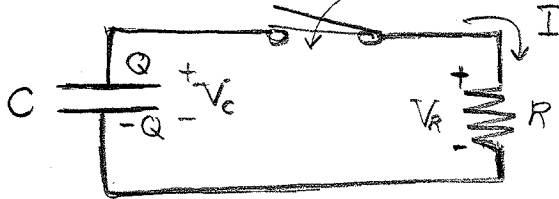


RC CIRCUITS:

We begin with the problem of discharging a capacitor C through a resistor R . Assume the capacitor has charge $Q(t)$ at time t . In particular $Q(0) = Q_0$.

ES7



close switch
at $t = 0$

$$I_0 = \frac{V_0}{R} = \frac{Q_0}{RC} \quad (\text{current at } t = 0)$$

$$I = -\frac{dQ}{dt}$$

(minus because charge is leaving the capacitor and we're using the capacitor to index the charge)

Note also $V_c = V_R$


but $V_c = Q/C$ whereas $V_R = IR$,

$$\frac{Q}{C} = IR = -R \frac{dQ}{dt}$$

$$\Rightarrow \frac{dQ}{Q} = -\frac{dt}{RC}$$

$$\Rightarrow \ln|Q| = -\frac{t}{RC} + C_1$$
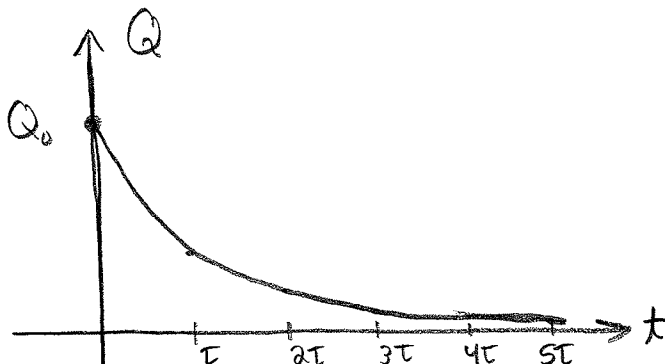
$$\Rightarrow \boxed{Q(t) = Q_0 \exp(-t/RC)}$$



$\tau = RC =$ time constant for circuit. After 5τ about 99% of Q_0 is discharged.

$\left(\lim_{t \rightarrow \infty} Q(t) = 0 \quad \underline{\text{BUT}} \quad Q(t) \neq 0 \quad \forall t \in \mathbb{R} \right)$

We found $Q(t) = Q_0 e^{-t/\tau}$ for $\tau = RC$

The current in the circuit is found by differentiation since $I = -dQ/dt$,



$$\begin{aligned}
 I(t) &= -\frac{d}{dt}(Q_0 e^{-t/\tau}) \\
 &= -Q_0 e^{-t/\tau} \frac{d}{dt}(-t/\tau) \\
 &= \boxed{\frac{Q_0}{RC} e^{-t/RC} = I(t)}
 \end{aligned}$$

We can also write the voltage across R and C,


$$V_R(t) = \begin{cases} 0 & : t < 0 \\ \frac{Q_0}{C} e^{-t/RC} & : t \geq 0 \end{cases}$$

$$V_C(t) = \frac{Q(t)}{C} = \begin{cases} \frac{Q_0}{C} & : t < 0 \\ \frac{Q_0}{C} e^{-t/RC} & : t \geq 0 \end{cases}$$

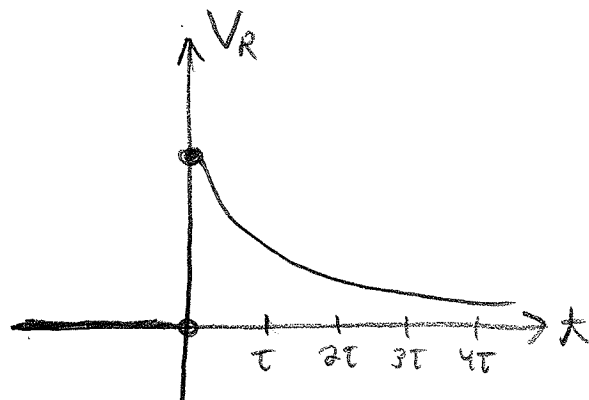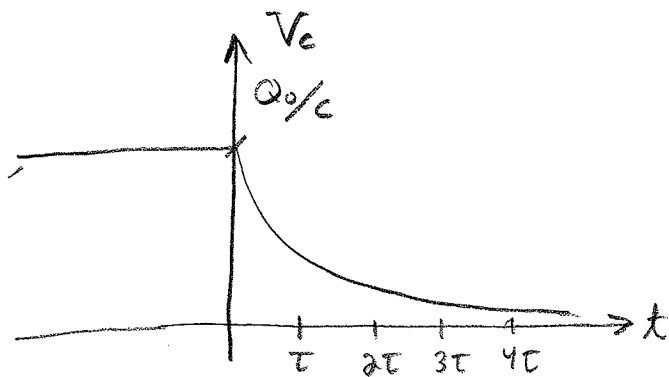Note: the voltage across R jumps at $t=0$, it is discontinuous. However, the V_C is continuous at $t=0$.



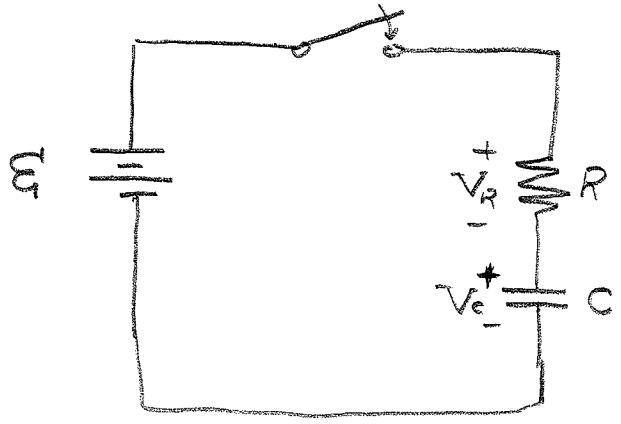E58) Close switch at $t=0$ and find current I and V_R and V_C as function of time for circuit pictured below



Let $Q(t)$ be charge on C at time t . Kirchhoff's Voltage Law around circuit yields:

$$\mathcal{E} - V_R - V_C = 0$$

$$V_R = IR \quad V_C = \frac{Q}{C}$$

Here $I > 0 \Rightarrow Q$ increases thus $I = \frac{dQ}{dt}$. We find that,

$$\mathcal{E} - R \frac{dQ}{dt} - \frac{Q}{C} = 0$$

Algebra $\Rightarrow \frac{dQ}{dt} + \frac{1}{RC} Q = \frac{\mathcal{E}}{R}$

Calculus $\Rightarrow \underline{Q(t) = k e^{-t/RC} + C \mathcal{E}}$. (I-factor method)

Now, $Q(0) = 0$ hence $Q(0) = k + C \mathcal{E}$ so we find $k = -C \mathcal{E}$ and hence,

$$Q(t) = C \mathcal{E} (1 - e^{-t/RC})$$



Continuing, now that we've calculated $Q(t)$ it's easy to find I , V_R and V_C .

$$V_C = \frac{Q}{C} = \frac{\mathcal{E}(1 - e^{-t/RC})}{C}, \text{ for } t \geq 0$$

Differentiate, $I = \frac{dQ}{dt}$,

$$I = \frac{d}{dt} [C \mathcal{E}(1 - e^{-t/RC})]$$

$$= -C \mathcal{E} \left(\frac{-1}{RC} e^{-t/RC} \right)$$

$$= \frac{\mathcal{E}}{R} e^{-t/RC}, \text{ for } t \geq 0$$

$$\text{Finally, } V_R = IR = \underline{\mathcal{E} e^{-t/RC} \text{ for } t \geq 0}$$

To summarize:

$$V_C(t) = \begin{cases} 0 & : t < 0 \\ \mathcal{E}(1 - e^{-t/RC}) & : t \geq 0 \end{cases}$$

No jump in V_C at $t=0$

$$V_R(t) = \begin{cases} 0 & : t < 0 \\ \mathcal{E} e^{-t/RC} & : t \geq 0 \end{cases}$$

↗ jumps at $t=0$

$$I(t) = \begin{cases} 0 & : t < 0 \\ \frac{\mathcal{E}}{R} e^{-t/RC} & : t \geq 0 \end{cases}$$

↘ jumps at $t=0$

Remark: CAPACITORS RESIST CHANGE IN VOLTAGE. SINCE $V_C = Q/C$ and instantaneous $\Delta V_C \Rightarrow$ instantaneous change in $Q \Rightarrow$ infinite current.